

ECE 337: ASIC Design

Lab 6

Simplified I²C Transmit-only Slave
Individual Mini-Design Project

Week of 9/23/2013



Down the road a bit: The Project

- Think of a design that is applicable for an ASIC (or a FPGA). **A microcontroller should not be adequate (no elevator controllers)**
- Think about a parallel design
- Blackboard contains past project ideas. Good ideas include protocol interfacing and signal processing... (no simple-math co-processors)
- Due to time limitations, a subset of a given protocol may be acceptable
- Work in groups of 3-4 **only in your lab section**
- See Project Idea Guidelines posted online (due next Friday), you are encouraged to submit multiple ideas.



Lab 6 High-Level

- Will be designing a simplified I²C Transmit-only Slave
- Two-week, **individual lab**
- Two main phases with optional source grade check
 - Preparation Diagrams
 - Due by end of 4th TA office hours after your lab
 - Phase 1: Sub-block code & test benches
 - Due late night the day of your lab next week
 - Optional complete source only grade submission
 - 48 hours prior to Phase 2 deadline
 - Phase 2: Complete mapped version
 - Start of Lab week after next (Week of 10/7)




Simplified I²C Slave Interface

- Transmit-only I²C Slave interface, subset of I²C Slave spec.
 - Transmits data to a master upon request
 - Takes data to transmit out of a FIFO
 - Higher level functions not handled for lab feasibility (Bus arbitration, multiple masters on the same bus, etc.)
- Uses separate buses for data and the data clock
 - SDA line is the data bus
 - SCL line is the data clock bus
- “Starting”/”Target” byte for a transmission
 - Contains address/id of target device
 - Contains the data transfer mode (read/write)
- Clock synchronization (using data transitions)
- Real I²C includes “clock-stretching” (we won’t)
 - used to supply flow control feedback from a slave to a master
- Uses START conditions to signal the start of a transmission
- Uses a STOP condition to signal the end of a transmission
- Transmit Data written to FIFO Queue from interface to external device (provided)


I²C Bus Characteristics

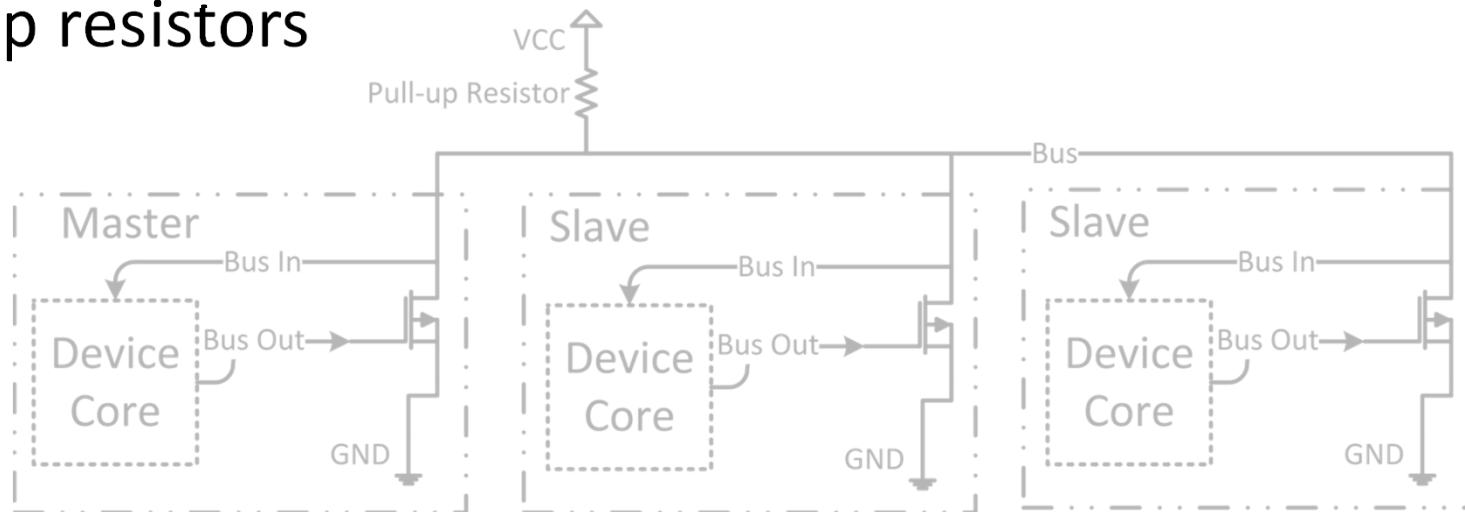- Each wire (SDA, SCL) is a bi-directional bus
- Each wire (SDA, SCL) operates with a 0's priority
 - 0's override 1's if written to the bus simultaneously
- Implemented using open-drain connections with pull-up resistors




Start Condition

 - High to low transition on the SDA Line while the SCL line is high
- Signals the start of a new transmission
(wakes up all slaves)




Starting/Target Byte

 - The first byte sent following a START condition
- Must be acknowledged by the identified slave to start transfer, otherwise transmission is terminated
- Read/Write mode is from the perspective of the master
 - Read: Master reads from bus/Slave writes to bus
 - Write: Master writes to bus/Slave reads from bus



STOP Condition

 - Low to High transition on the SDA line while SCL line is high
- Signals the end of a transmission






Complete Transmission

1. Begins with START Condition, followed by a “Starting” byte
2. Identified Slave acknowledges (ACK) the master
3. The slave sends data byte from FIFO
4. The slave checks for ACK from Master
5. Repeat steps 3 & 4 until master not-acknowledges (NACK)
6. Transmission is done
 - Need to hold on to last data byte for a retransmission/future transmission requested by the master.

System Overview

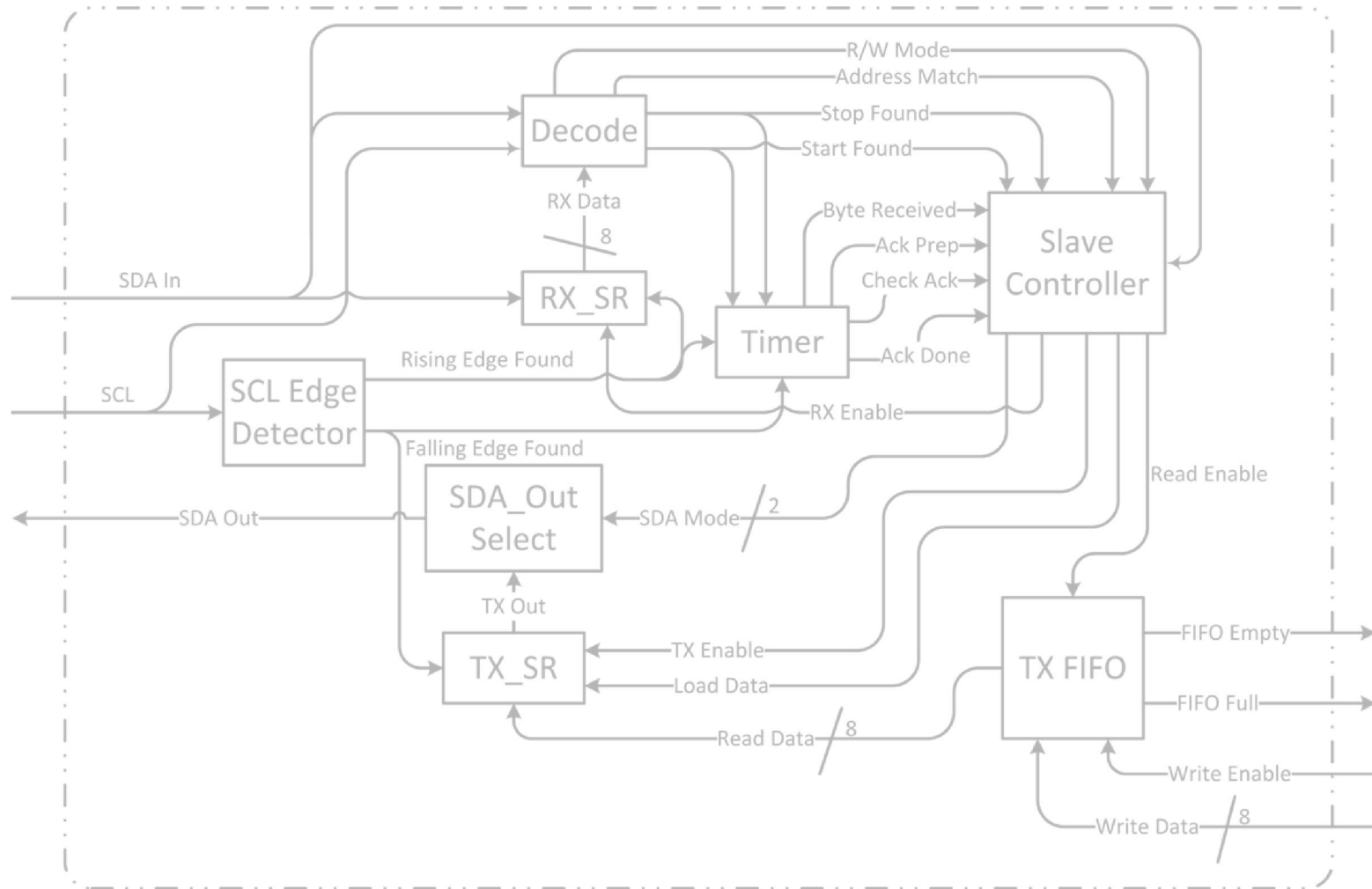

TX FIFO

- The FIFO is **provided**, you need to make a “wrapper” file.
- FIFO writes data from write_data on a clock edge, while write_enable is high.
- FIFO outputs data on read_data, increments to next byte when read_enable is high and there is a clock edge.
- fifo_full and fifo_empty indicate FIFO status
- Provided FIFO has two clocks
 - Why? This FIFO was designed to provided interface between circuits running on different clocks
 - you will tie them to same system clock

Simulating the Open-drain buses

- Use the provided i2c_bus module
 - Connect your slave design to it
 - Connect the test bench's emulated master signals to it
- It will implement and enforce all of the open-drain & pull-up resistor characteristics
- It has assertions to check if multiple devices are trying to drive the bus low
- You can view what happens to the bus by adding the internal signals (bi_dir_sda & bi_dir_scl)

